

EE671: VLSI Design

Assignment 4

Saksham Gupta, 20D170037

October 21, 2022

Abstract

Your abstract.

1 Elemental Logic Blocks

Roll No. - 20D170037

Last Digit - 7

AND - 47ps

XOR - 64ps

$A+B.C$ - 74ps

$A.B + C.(A+B)$ - 74ps

1.1 RTL Views:

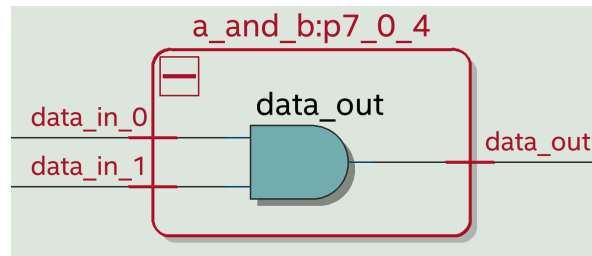


Figure 1: AND Logic Function

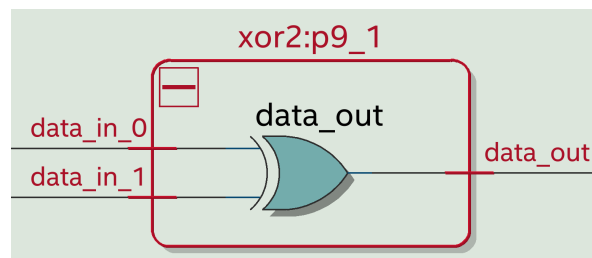


Figure 2: XOR Logic Function

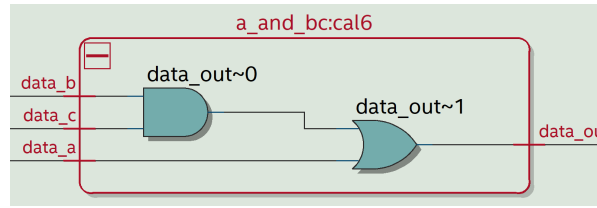


Figure 3: $A + B.C$ Logic Function

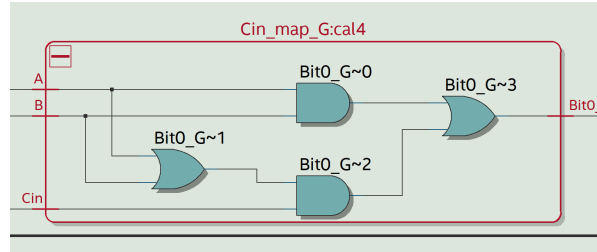


Figure 4: $A.B + C.(A+B)$ Logic Function

2 Further Procedure

- We generate the various orders of G and P values using the logic blocks in the previous part
- We write the VHDL code that reads a pair of 16-bit numbers and single bit input carry, and generates the expected 16-bit sum and 1 bit output carry using a Brent Kung Adder
- The Brent Kung adder defined using VHDL, is simulated using ModelSim considering 32 randomly chosen pairs of 16-bit numbers and 1-bit input carry


```

-- Note: SUCCESS, all tests passed.
# Time: 1280 ns Iteration: 0 Instance: /testbench

```

Figure 5: ModelSim window after performing simulation

3 Output Waveform

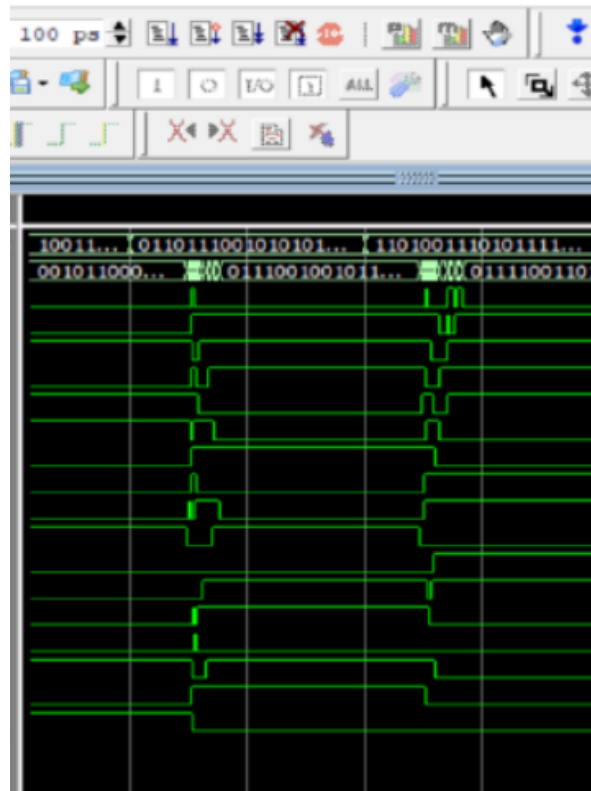

VHDL CODE FOR ALL IS PROVIDED ALONG WITH THE SUBMISSION